

Applying the Wheatstone Bridge Circuit



measurement with confidence

Dirk Eberlein
dirk.eberlein@hbm.com

www.hbm.com

The relationship between the applied strain ε and the relative change of the resistance of a strain gauge

A strain gauge converts a mechanical strain into a change of an electrical resistance.

“gauge factor”:

characteristic of the strain gauge and has to be checked experimentally:

$$\frac{\Delta R}{R} = k \cdot \varepsilon$$

Applying the Wheatstone Bridge Circuit



Test of the gauge factor



Thomas Kleckers, HBM

Value of the relative change of the resistance

$$\Delta R/R_0 = k \cdot \varepsilon$$

$$k \sim 2 \quad R_{(\text{typ.})} = 120\Omega \text{ or } 350\Omega$$

$\varepsilon \longrightarrow$ for example – (strain level for transducers)


 $1000 \mu\text{m/m} = 1\text{mm/m} (0,1\%)$

E.g.: 120Ω -strain gauge at $1\text{mm/m} = 0,24\Omega$ change of the resistance


 Measurements with an ohmmeter are impossible

Basics
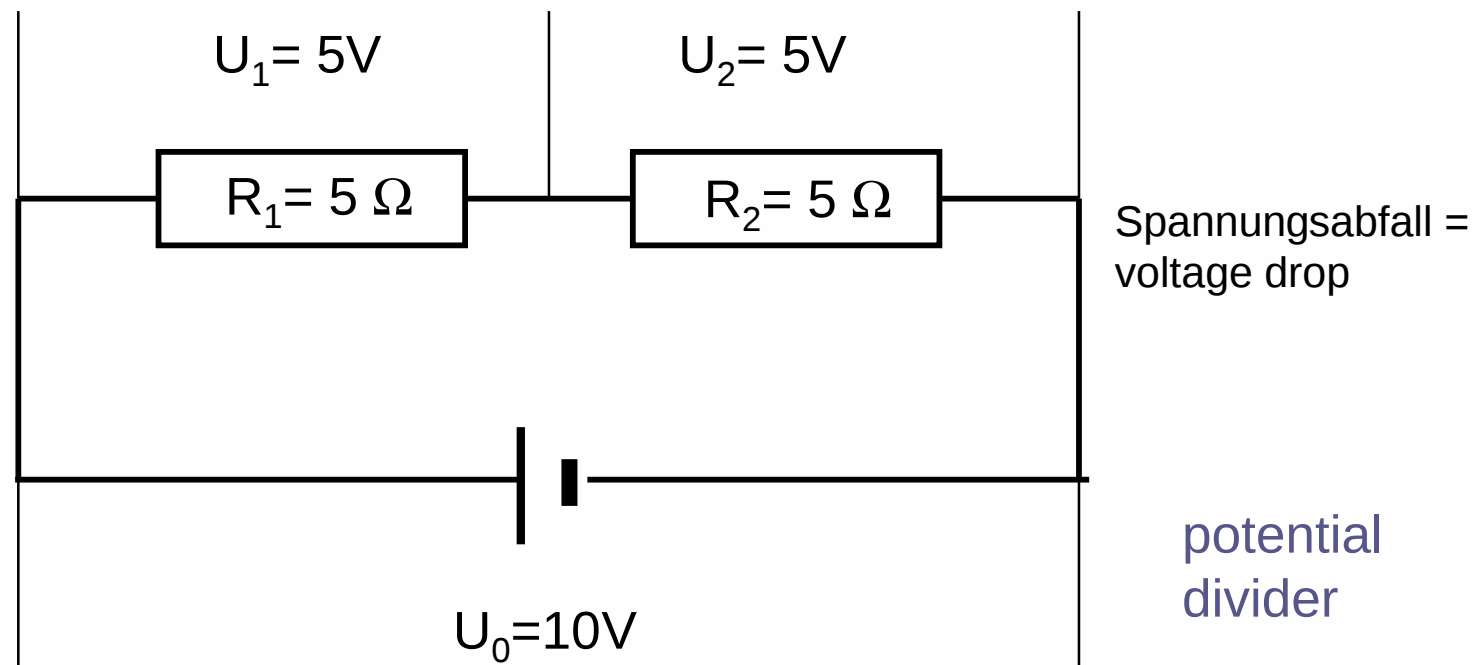
$$\frac{U_1}{U_0} = \frac{R_1}{R_1 + R_2} \quad \rightarrow \quad U_1 = U_0 \frac{R_1}{R_1 + R_2}$$



Basics

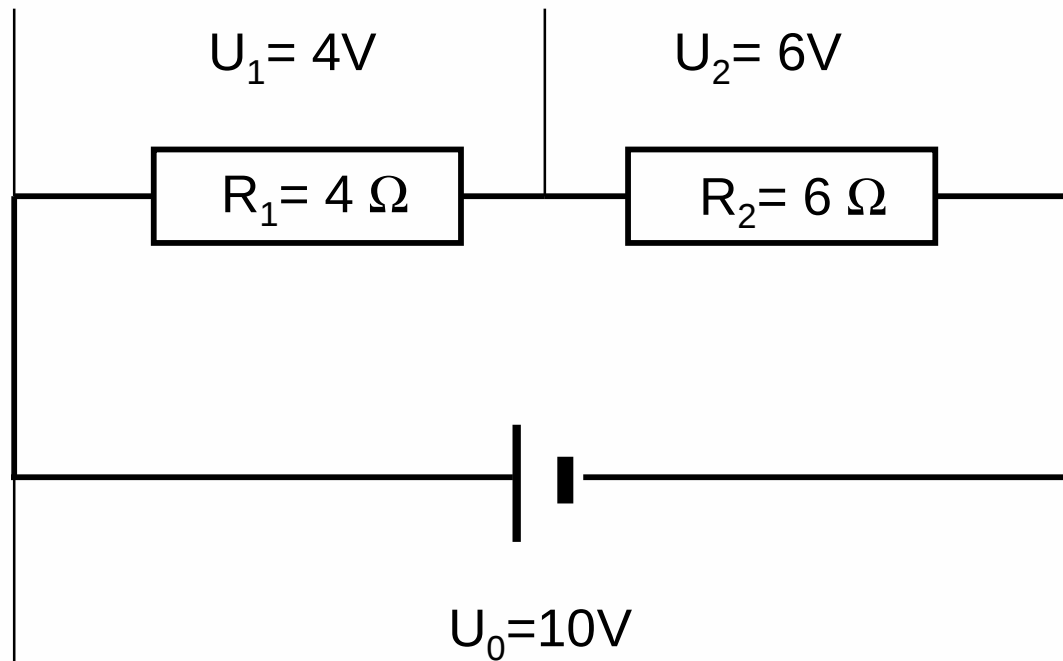


$$\frac{U_1}{U_0} = \frac{R_1}{R_1 + R_2} \quad \Rightarrow \quad U_1 = U_0 \frac{R_1}{R_1 + R_2}$$


potential
divider

Applying the Wheatstone Bridge Circuit

Basics

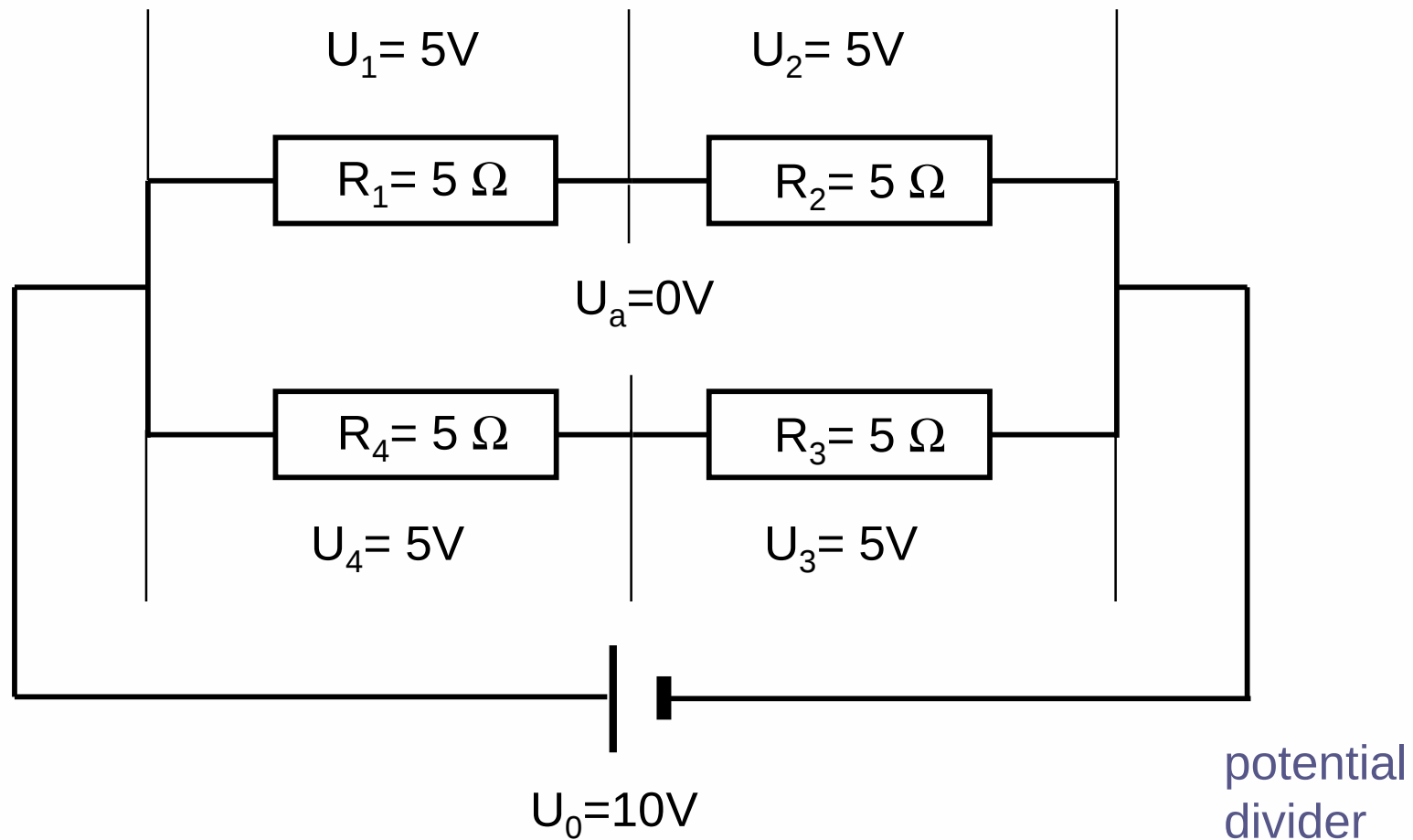


Basics

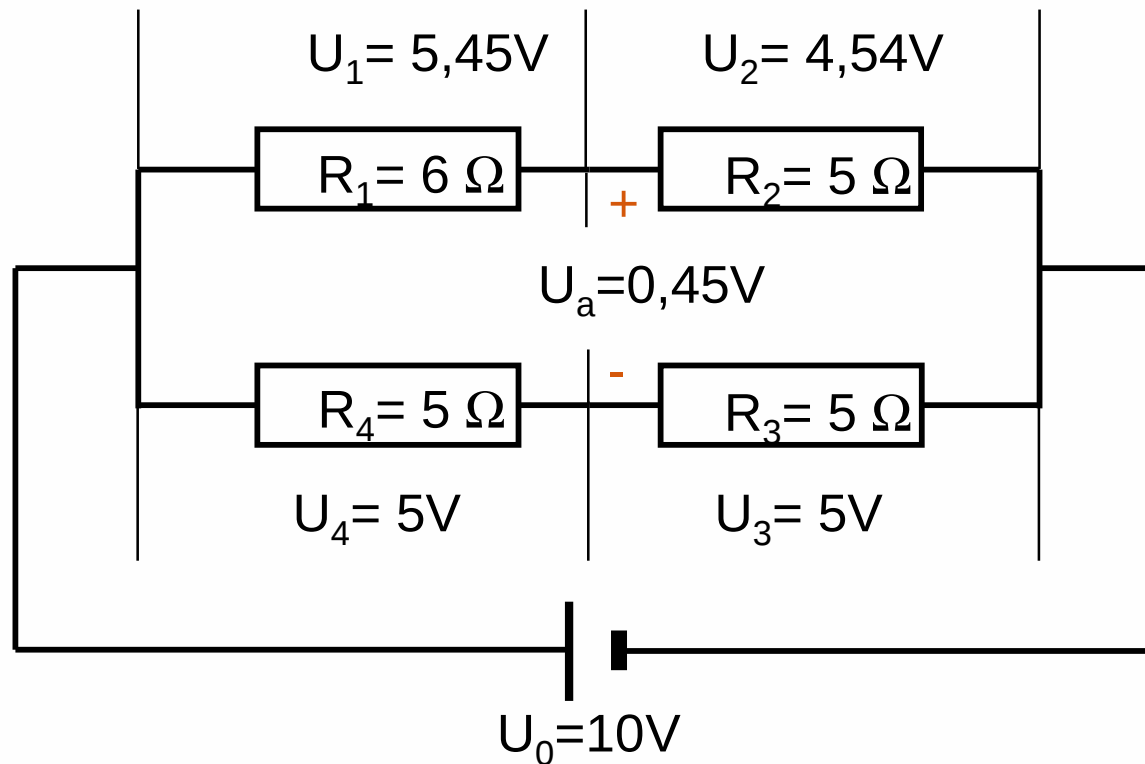

increasing of R_1 $\longrightarrow$ output voltage U_a will be positive

decreasing of R_1 $\longrightarrow$ output voltage U_a will be negative


Basics

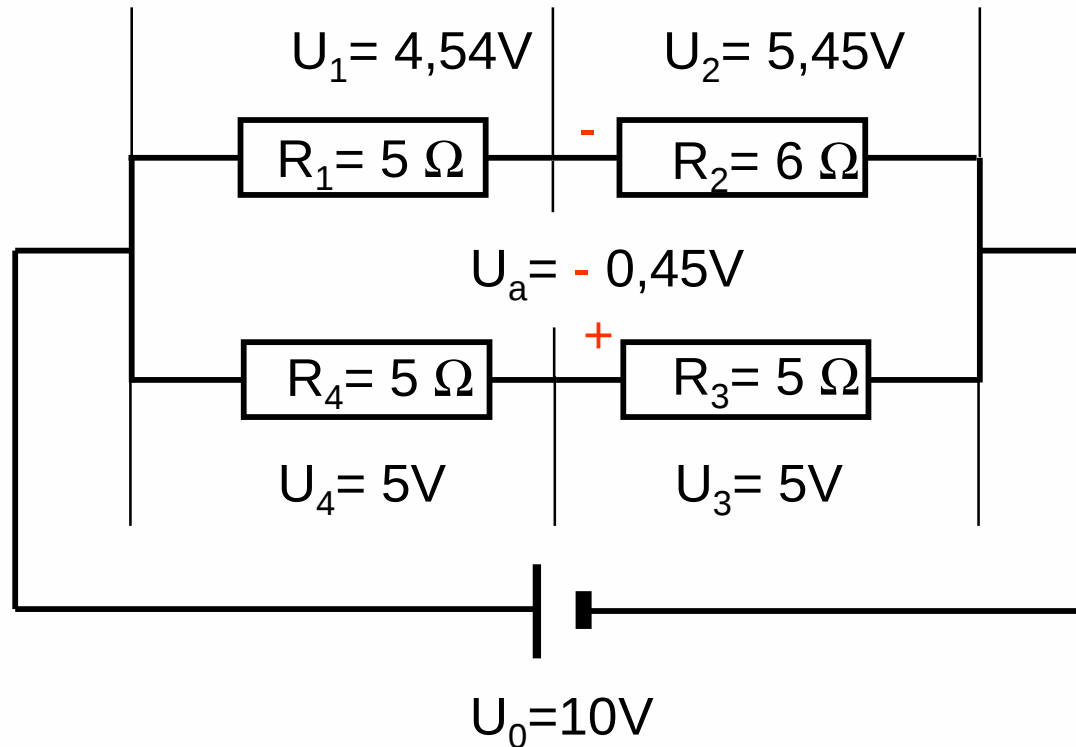

increasing of R_2 $\longrightarrow$ output voltage U_a will be negative

decreasing of R_2 $\longrightarrow$ output voltage U_a will be positive

Basics

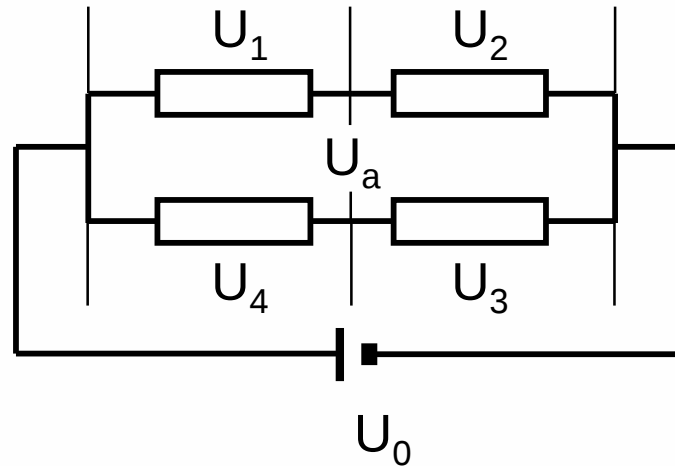

$$U_1 = U_0 \frac{R_1}{R_1 + R_2}$$

$$U_4 = U_0 \frac{R_4}{R_3 + R_4}$$

$$U_a = U_0 \left(\frac{R_1}{R_1 + R_2} - \frac{R_4}{R_3 + R_4} \right)$$

$$U_a = U_0 \left(\frac{R_1 + \Delta R_1}{R_1 + \Delta R_1 + R_2 + \Delta R_2} - \frac{R_4 + \Delta R_4}{R_3 + \Delta R_3 + R_4 + \Delta R_4} \right)$$

Basics

$$U_a = U_0 \left(\frac{R_1 + \Delta R_1}{R_1 + \Delta R_1 + R_2 + \Delta R_2} - \frac{R_4 + \Delta R_4}{R_3 + \Delta R_3 + R_4 + \Delta R_4} \right)$$

the resistance changes in the strain gauges are very small :

$$\Delta R \ll R$$

the two halves of the bridge must have the same resistance:

$$R_1 = R_2 \text{ und } R_3 = R_4$$

Basics

$$\frac{U_a}{U_0} = \frac{\Delta R_1}{R_1} - \frac{\Delta R_2}{R_2} + \frac{\Delta R_3}{R_3} - \frac{\Delta R_4}{R_4}$$

with:


$$\frac{\Delta R}{R} = k \cdot \varepsilon \quad \text{that implies:}$$

$$\frac{U_a}{U_0} = \frac{k}{4} \cdot (\varepsilon_1 - \varepsilon_2 + \varepsilon_3 - \varepsilon_4)$$

Basics

- we use every time the Wheatstone Bridge Circuit with 4 resistors
- these 4 resistors could be 1, 2 or 4 strain gauges
- modern amplifiers completing “missing” resistors in the Wheatstone Bridge Circuit
- with 4 active strain gauges we get the largest output value



Basics

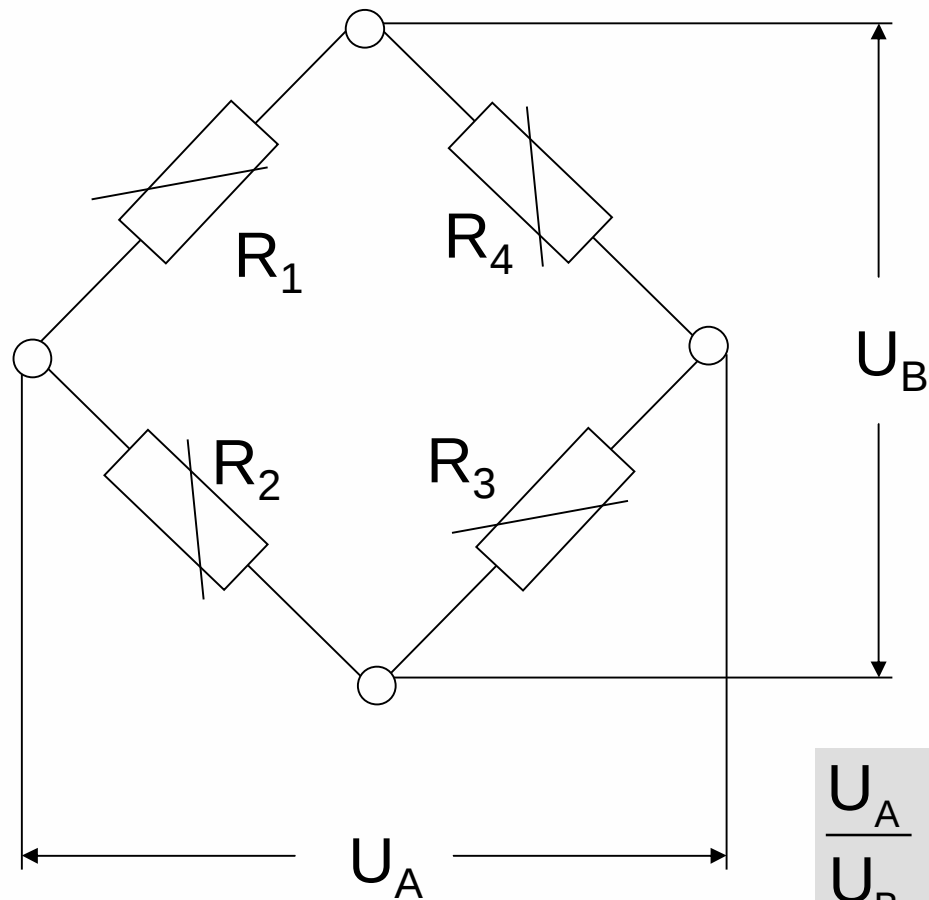


$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$

Elementary circuits with strain gauges


Quarter bridge **1 active** strain gauge

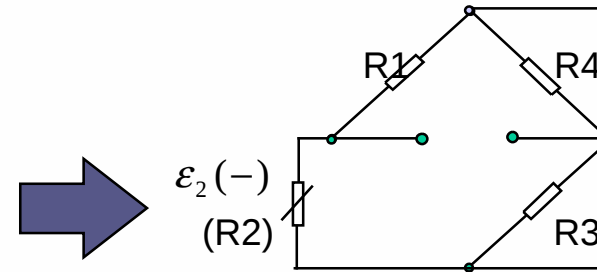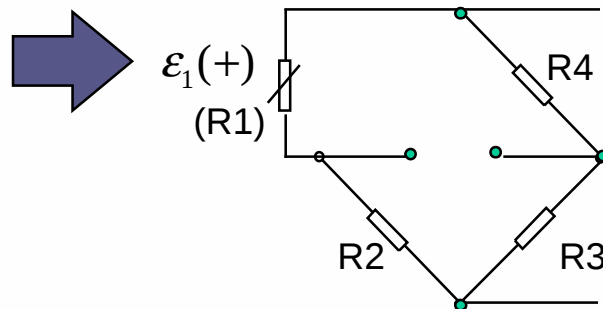


Half bridge **2 active** strain gauges

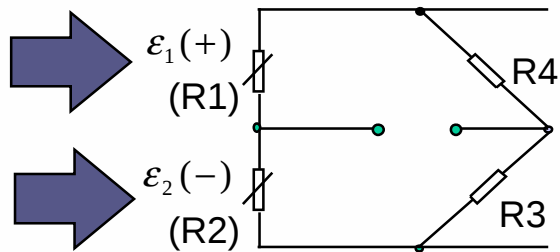

Full bridge **4 active** strain gauges

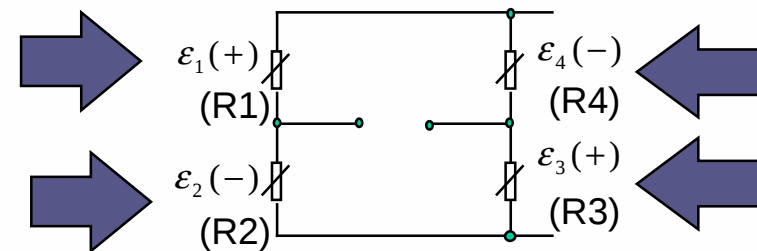

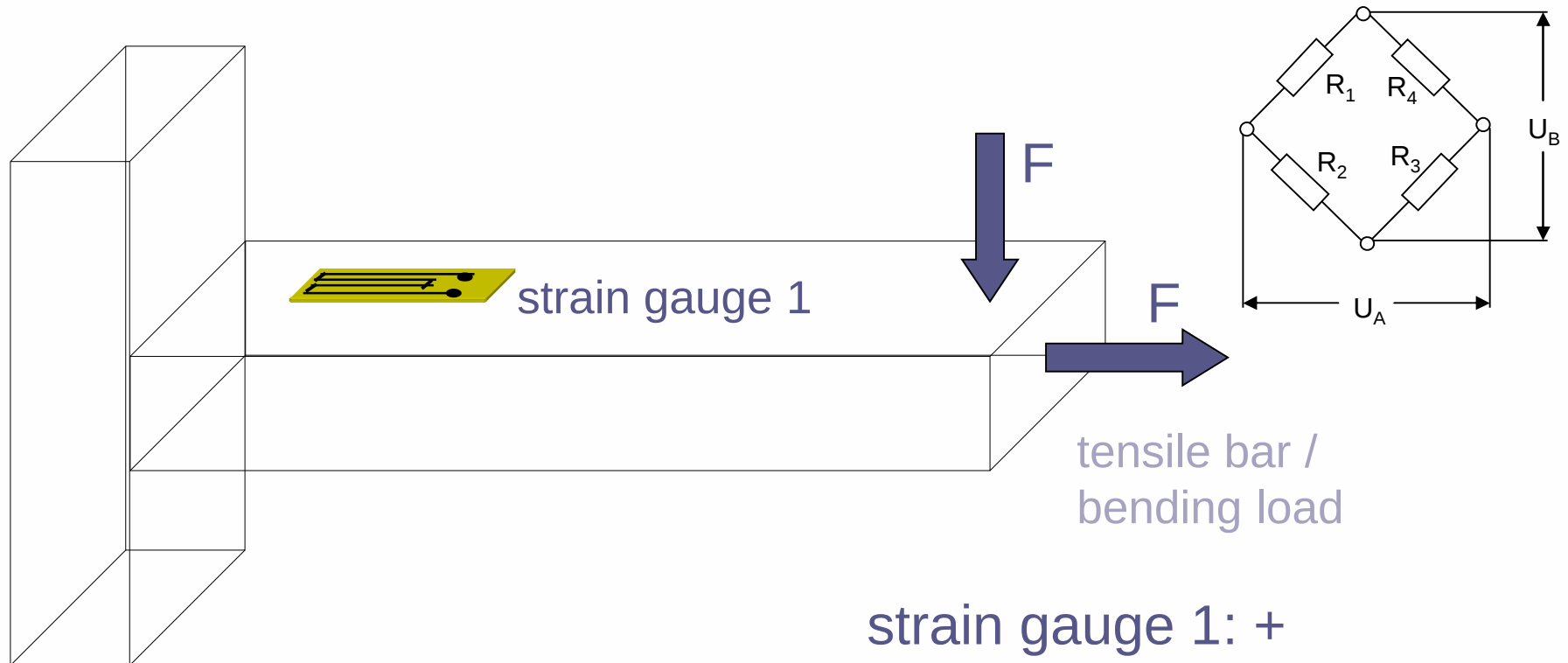Measurements on a bending beam (Quarter Bridge)



$$\frac{U_A}{U_B} = \frac{k}{4}(\epsilon_1)$$

Temperature compensation: No!

Calibrating measurement equipment (Quarter Bridge)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2 + \varepsilon_3 - \varepsilon_4)$$

$k = 2$ **gauge factor** (written on the strain gauge package)


estimated strain level $\varepsilon = 1000 \mu\text{m/m}$ (**estimation!**)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \cancel{\varepsilon_2} + \cancel{\varepsilon_3} - \cancel{\varepsilon_4})$$

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1) = \frac{2}{4} (1000 \mu\text{m/m}) = 0,5 \cdot 1000 \cdot 10^{-6} = 0,5 \cdot 10^{-3}$$

$$\underline{\underline{\frac{U_A}{U_B} = 0,5 \text{mV/V}}}$$

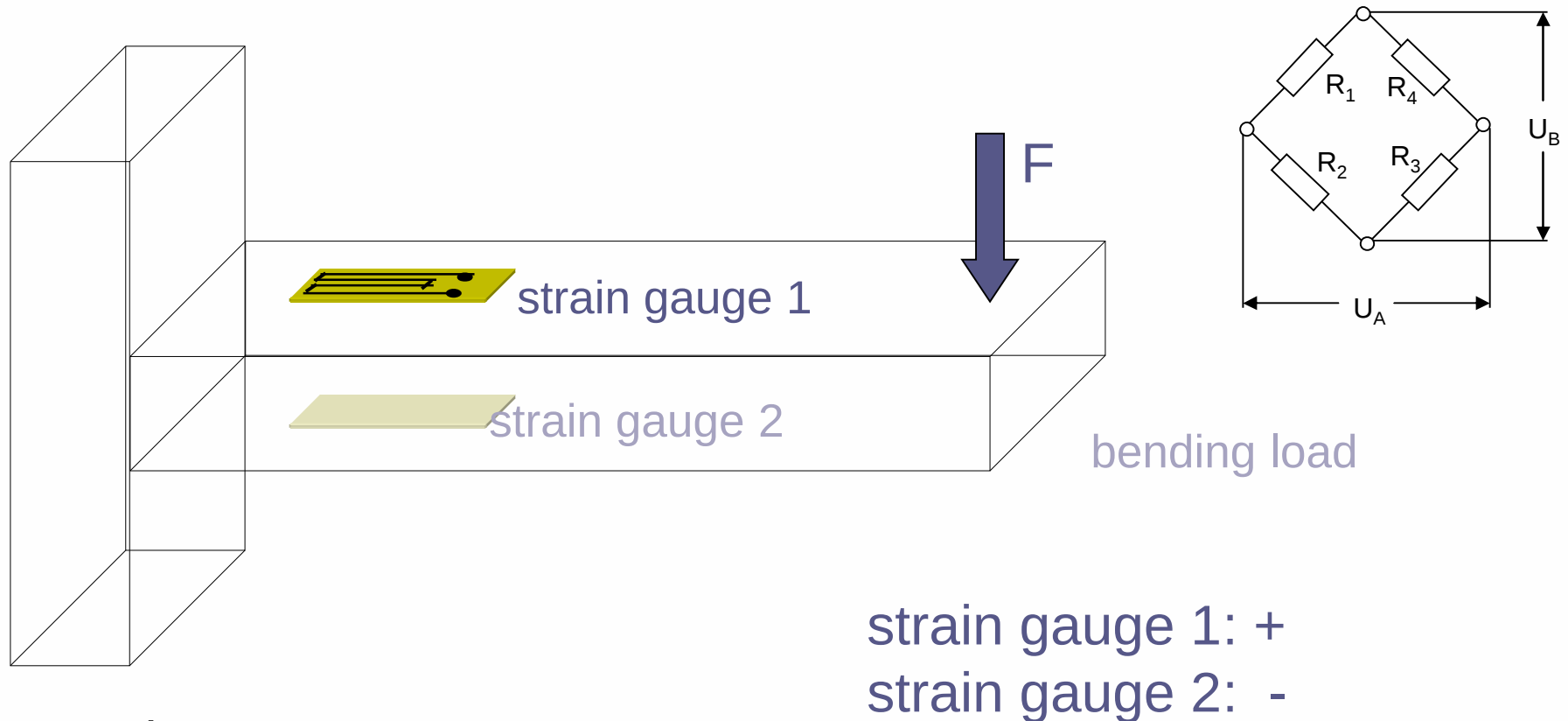
Measurements on a bending beam (Half Bridge)



$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2)$$

Temperature compensation: Yes!

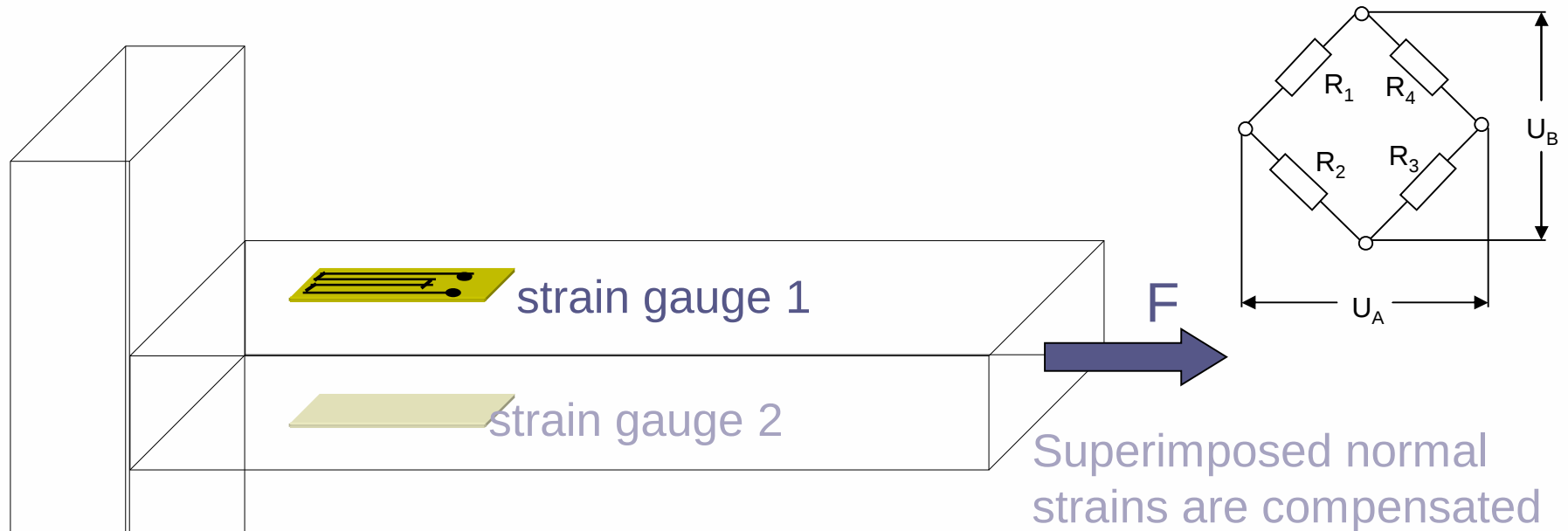Measurements on a bending beam (Half Bridge)



strain gauge 1: +
strain gauge 2: +

$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2)$$

Temperature compensation: Yes!

Calibrating measurement equipment (Half Bridge)

$k = 2$ **gauge factor** (written on the strain gauge package)

estimated strain level $\varepsilon = 1000 \mu\text{m/m}$ (**estimation!**)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2 + \cancel{\varepsilon_3} - \cancel{\varepsilon_4})$$

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2) = \frac{2}{4} (1000 \mu\text{m/m} - [-1000 \mu\text{m/m}])$$

$$\frac{U_A}{U_B} = 0,5 \cdot 2000 \cdot 10^{-6} = 1 \cdot 10^{-3}$$

$$\underline{\underline{\frac{U_A}{U_B} = 1 \text{ mV/V}}}$$


2 times the output
value of a 1/4-bridge

Applying the Wheatstone Bridge Circuit



Optimisation of a wish mop

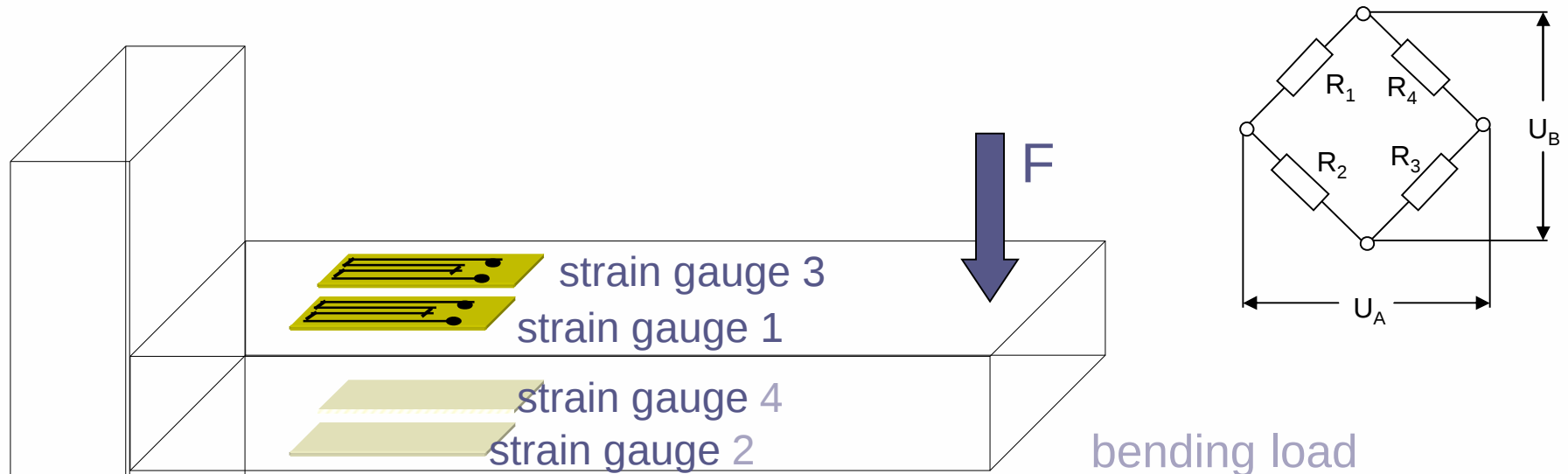Measurements on a bending beam (Full Bridge)




$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$

strain gauge 1: +
strain gauge 2: -
strain gauge 3: +
strain gauge 4: -

Temperature compensation: Yes!

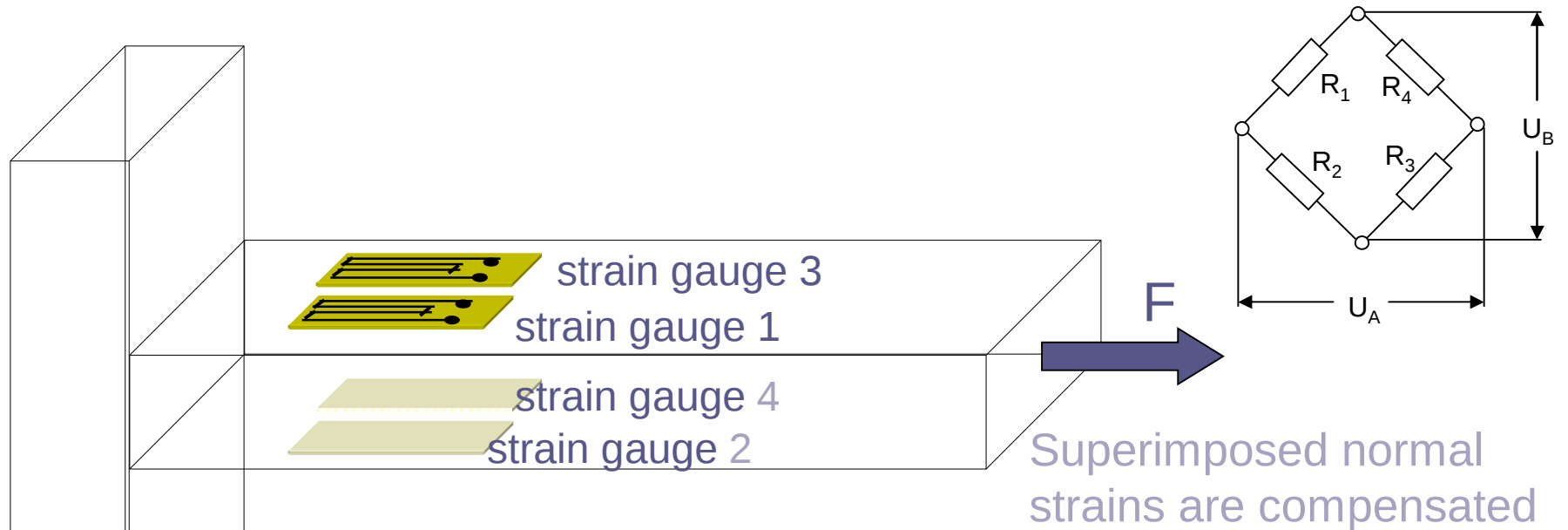Measurements on a bending beam (Full Bridge)



$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$

strain gauge 1: +
strain gauge 2: +
strain gauge 3: +
strain gauge 4: +

Temperature compensation: Yes!

Calibrating measurement equipment (Full Bridge)

$k = 2$ **gauge factor** (written on the strain gauge package)

estimated strain level $\varepsilon = 1000 \mu\text{m/m}$ (**estimation!**)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2 + \varepsilon_3 - \varepsilon_4)$$


$$\frac{U_A}{U_B} = \frac{2}{4} (1000 \mu\text{m/m} - [-1000 \mu\text{m/m}] + 1000 \mu\text{m/m} - [-1000 \mu\text{m/m}])$$

$$\frac{U_A}{U_B} = 0,5 \cdot 4000 \cdot 10^{-6} = 2 \cdot 10^{-3}$$

$$\underline{\underline{\frac{U_A}{U_B} = 2 \text{ mV/V}}}$$

4 times the output
value of a 1/4-bridge


... and the right strain gauge for this application

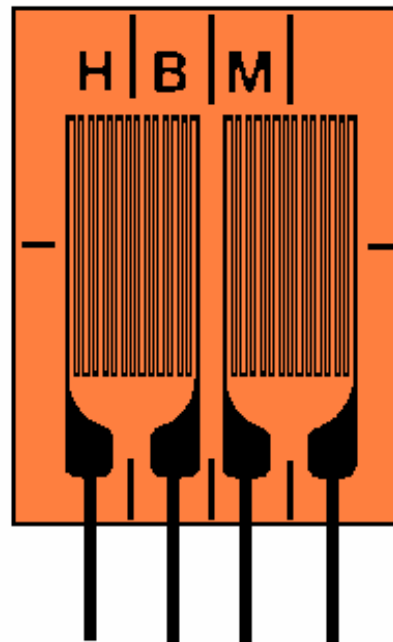

DY11...

Measurements on a tension/compression bar

(Half Bridge)

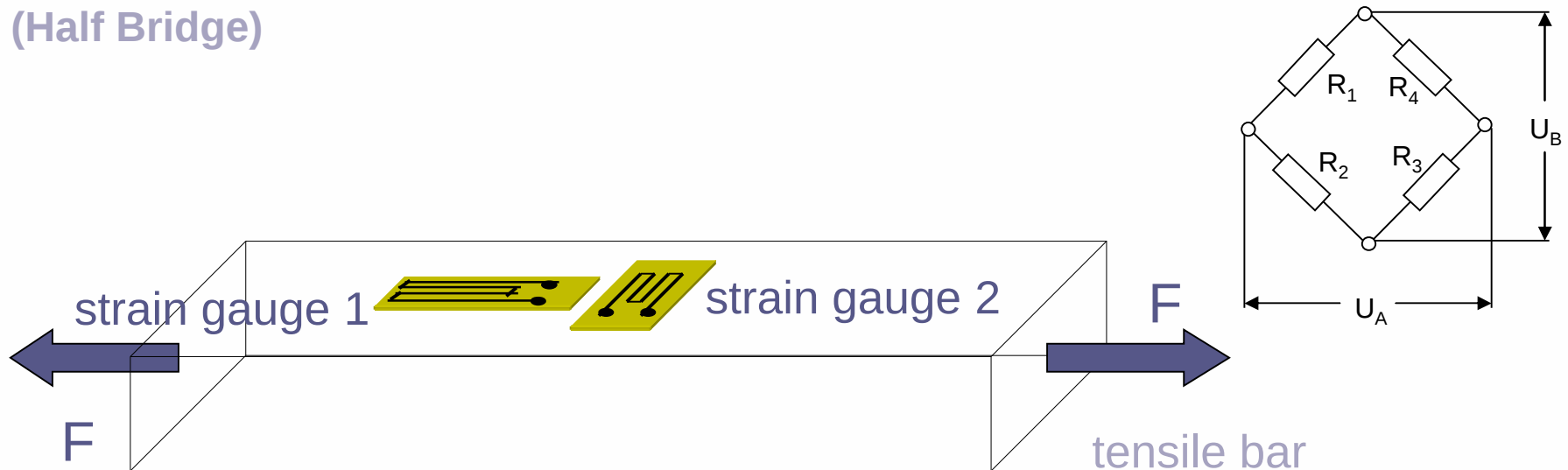

$$-v = \frac{\epsilon_q}{\epsilon_l} \Rightarrow \epsilon_q = -v\epsilon_l \Rightarrow \epsilon_2 = -v\epsilon_1$$

v ... Poisson's ratio (steel $\approx 0,3$)



$$\frac{U_A}{U_B} = \frac{k}{4}(\epsilon_1 - \epsilon_2) = \frac{k}{4}[\epsilon_1 - (-v\epsilon_1)]$$

strain gauge 1: +
strain gauge 2: -

Temperature compensation: Yes!

Measurements on a tension/compression bar

(Half Bridge)

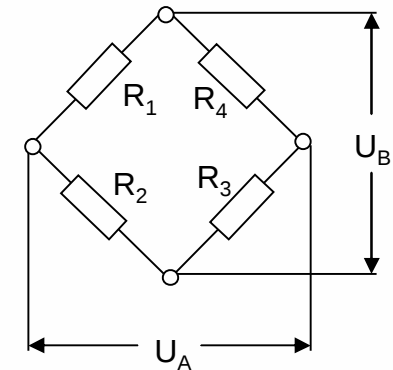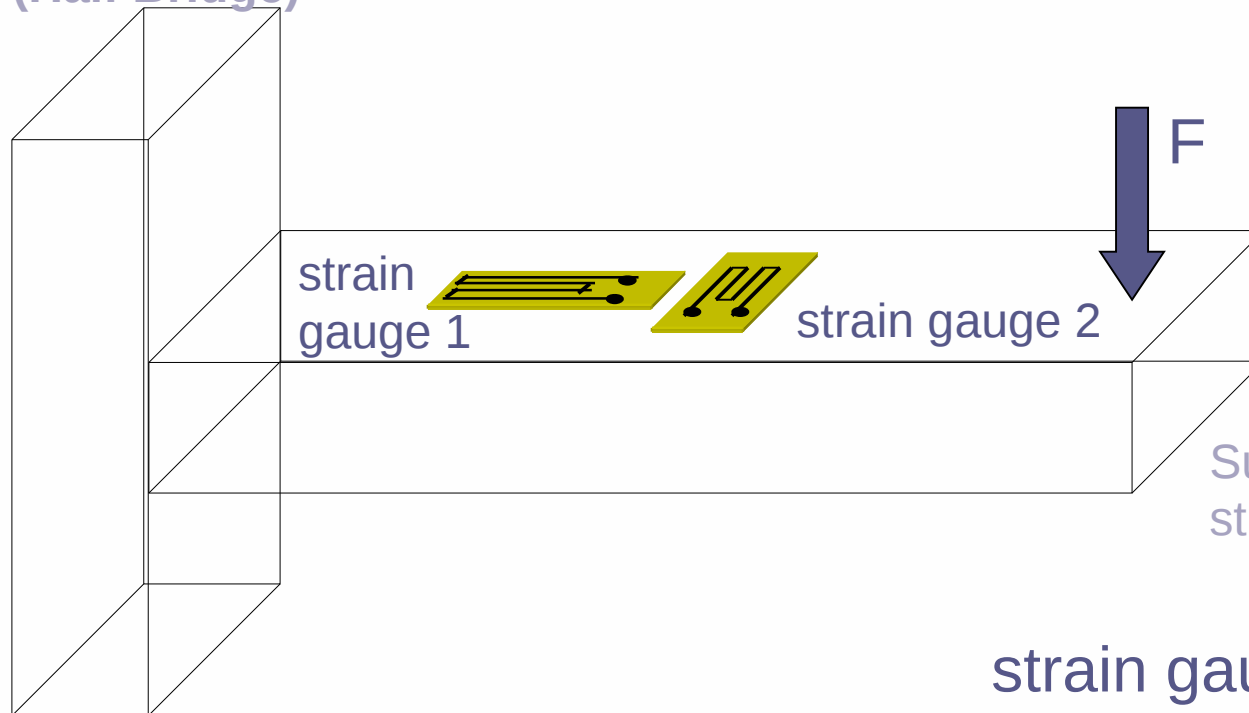

Superimposed bending strains occur in the result

strain gauge 1: +
strain gauge 2: -

$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2) = \frac{k}{4} [\epsilon_1 - (-\nu \epsilon_1)]$$

Temperature compensation: Yes!

Calibrating measurement equipment (Half Bridge)

$$k = 2; \nu = 0,3$$

estimated strain level $\varepsilon = 1000 \mu\text{m/m}$ (estimation!)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2 + \cancel{\varepsilon_3} - \cancel{\varepsilon_4})$$

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2) = \frac{k}{4} [\varepsilon_1 - (-\nu\varepsilon_1)] = \frac{2}{4} (1000\mu\text{m/m} - [-0,3 \cdot 1000\mu\text{m/m}])$$


$$\frac{U_A}{U_B} = 0,5 \cdot (1000\mu\text{m/m} - [-300\mu\text{m/m}]) = 0,5 \cdot 1300 \cdot 10^{-6} = 0,65 \cdot 10^{-3}$$

$$\underline{\underline{\frac{U_A}{U_B} = 0,65 \text{ mV/V}}}$$

1.3 times the output
value of a 1/4-bridge

Measurements on a tension/compression bar

(Full Bridge)

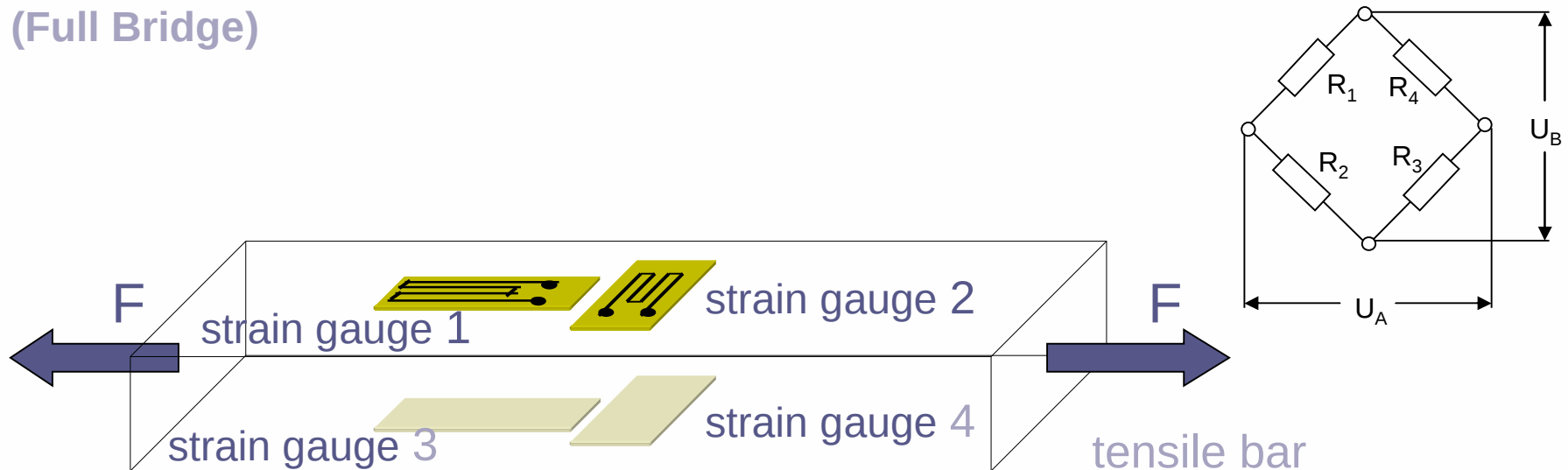

$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$



$$\frac{U_A}{U_B} = \frac{k}{4} [\epsilon_1 - (-\nu\epsilon_1) + \epsilon_3 - (-\nu\epsilon_3)]$$

strain gauge 1: +
strain gauge 2: -
strain gauge 3: +
strain gauge 4: -

Temperature compensation: Yes!

Measurements on a tension/compression bar

(Full Bridge)

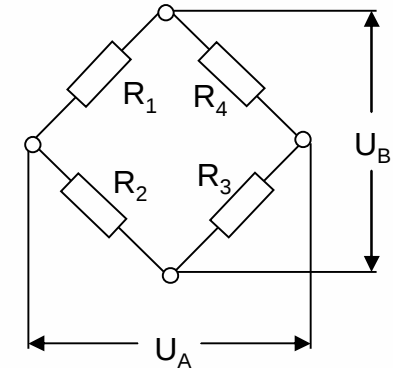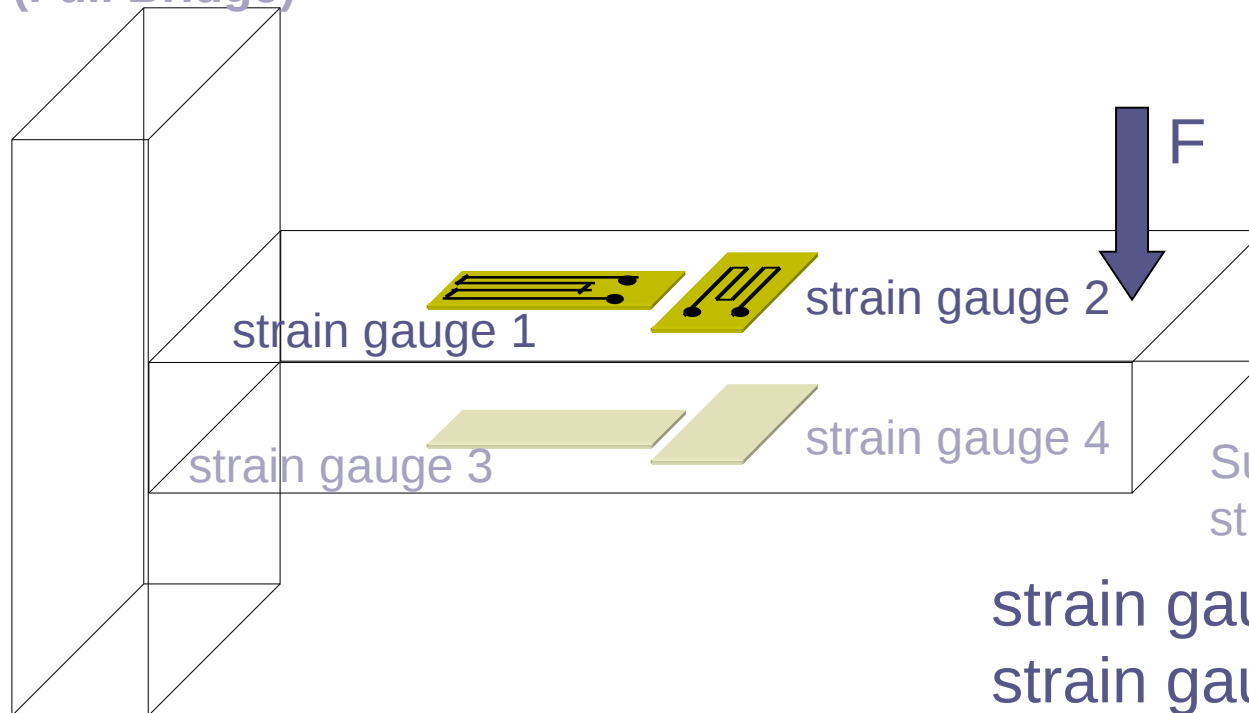

Superimposed bending strains are compensated

strain gauge 1: +
strain gauge 2: -
strain gauge 3: -
strain gauge 4: +

$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$

Calibrating measurement equipment (Full Bridge)

$$k = 2; \nu = 0,3$$

estimated strain level $\varepsilon = 1000 \mu\text{m/m}$ (estimation!)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2 + \varepsilon_3 - \varepsilon_4)$$


$$\frac{U_A}{U_B} = \frac{k}{4} [\varepsilon_1 - (-\nu\varepsilon_1) + \varepsilon_3 - (-\nu\varepsilon_3)]$$

$$\frac{U_A}{U_B} = \frac{2}{4} (1000\mu\text{m/m} - [-0,3 \cdot 1000\mu\text{m/m}] + 1000\mu\text{m/m} - [-0,3 \cdot 1000\mu\text{m/m}])$$


$$\frac{U_A}{U_B} = 0,5 \cdot 2600 \cdot 10^{-6} = 13 \cdot 10^{-3} = \underline{\underline{13 \text{ mV/V}}}$$

2.6 times the output
value of a 1/4-bridge

... and the right strain gauge for this application


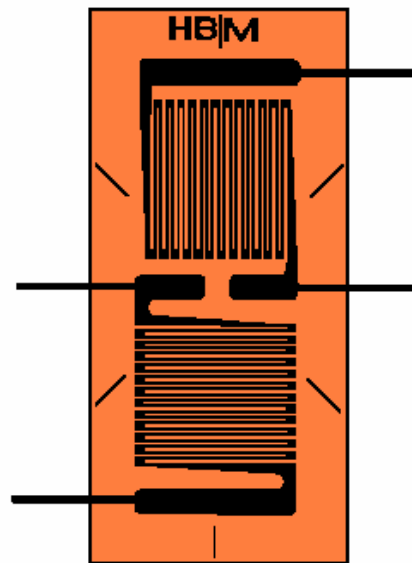


XY11...

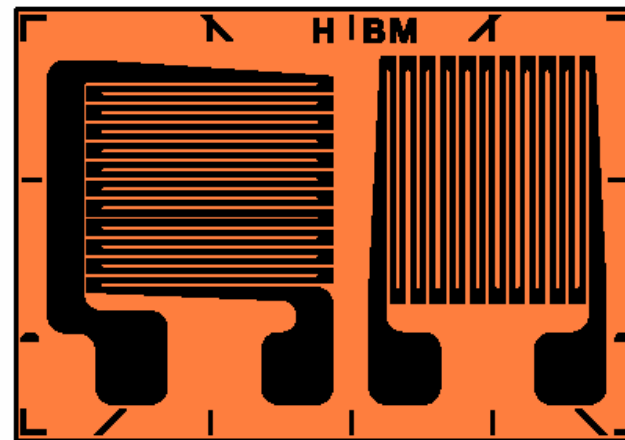

XY31...

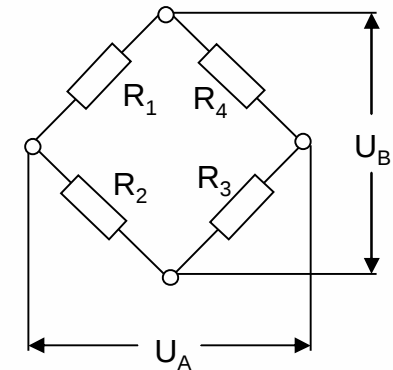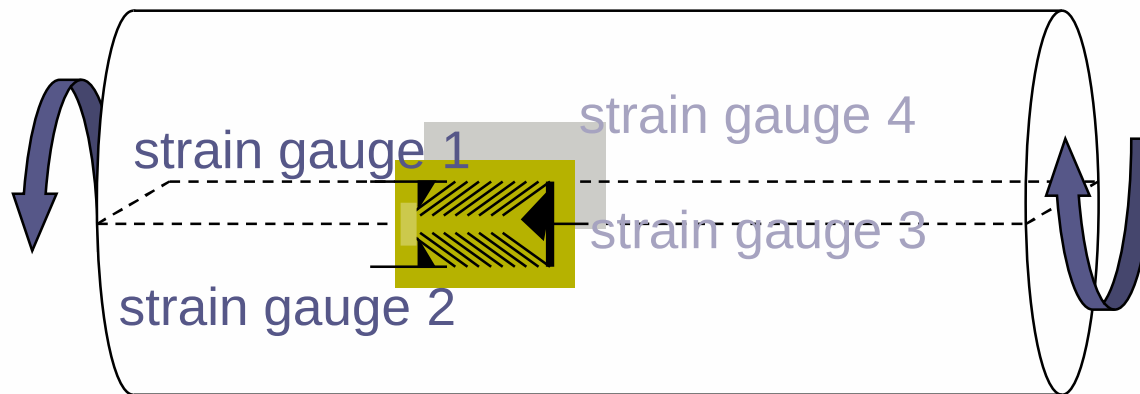Measurements on a shaft under torsion (Full Bridge)




Torsion shaft

strain gauge 1: +
strain gauge 2: -
strain gauge 3: +
strain gauge 4: -

$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$

Temperature compensation: Yes!

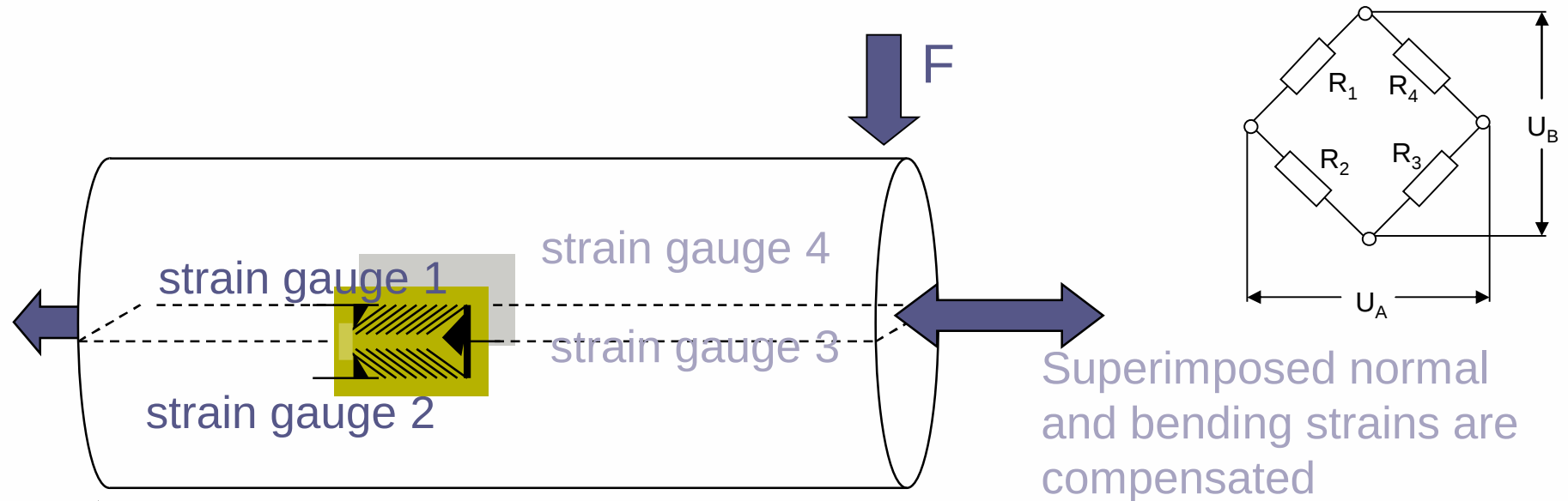Measurements on a shaft under torsion (Full Bridge)



strain gauge 1: +
strain gauge 2: -
strain gauge 3: -
strain gauge 4: +

$$\frac{U_A}{U_B} = \frac{k}{4} (\epsilon_1 - \epsilon_2 + \epsilon_3 - \epsilon_4)$$

Temperature compensation: Yes!

Calibrating measurement equipment (Full Bridge)

$$k = 2$$

estimated strain level $\varepsilon = 1000 \mu\text{m/m}$ (estimation!)

$$\frac{U_A}{U_B} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2 + \varepsilon_3 - \varepsilon_4)$$


$$\frac{U_A}{U_B} = \frac{2}{4} (1000\mu\text{m/m} - [-1000\mu\text{m/m}] + 1000\mu\text{m/m} - [-1000\mu\text{m/m}])$$

$$\frac{U_A}{U_B} = 0,5 \cdot 4000 \cdot 10^{-6} = 2 \cdot 10^{-3}$$


$$\underline{\underline{\frac{U_A}{U_B} = 2 \text{ mV/V}}}$$

4 times the output
value of a 1/4-bridge

... and the right strain gauge for this application

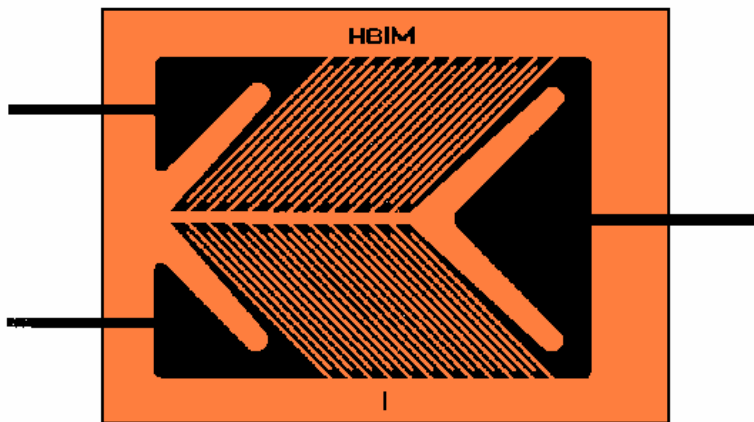

XY11...

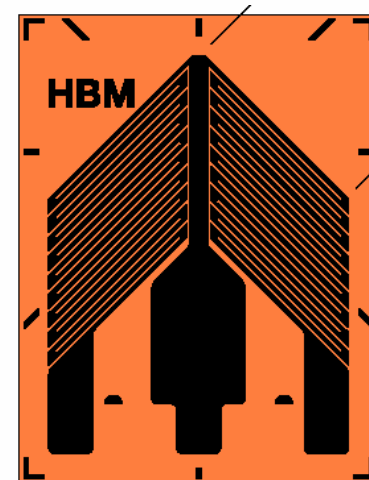


XY31...

strain gauge rosettes for stress analysis

two basic shapes (geometries):

$0^\circ/45^\circ/90^\circ$ -rosettes


$0^\circ/60^\circ/120^\circ$ -rosettes

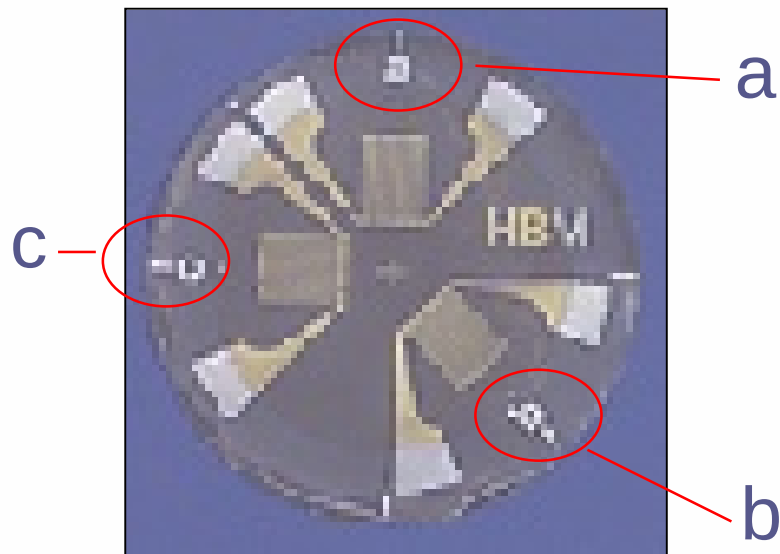

strain measurement in
3 directions (a, b, c)

strain gauge rosettes for stress analysis

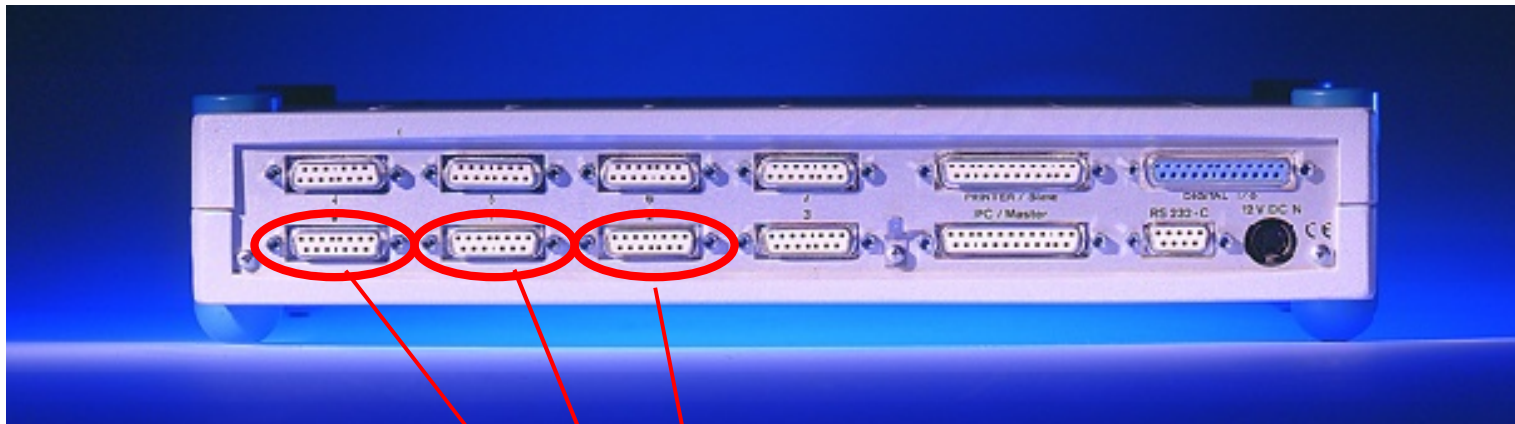Connection at the amplifier always as three different quarter bridges!




measuring grid a, b, c

e.g. Spider8-30

Calibrating measurement equipment

(3 different quarter bridges)

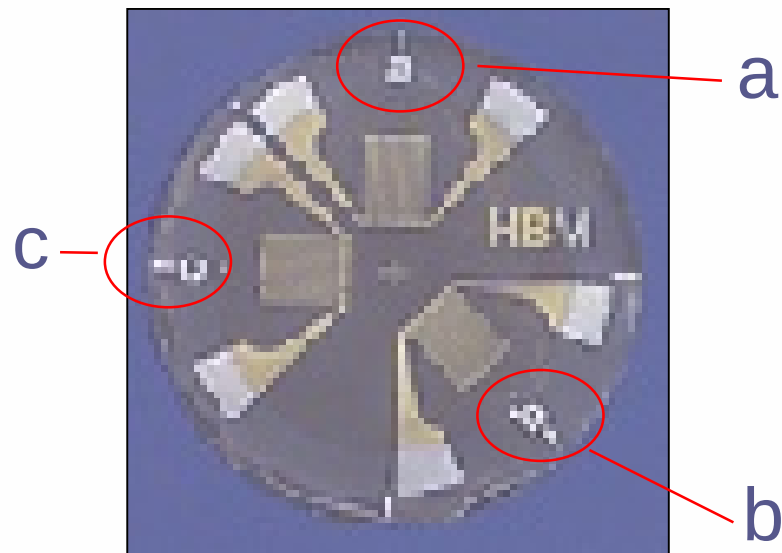
1000 $\mu\text{m}/\text{m}$ correspond to 2mV/V (at a gauge factor of 2),
valid for amplifier channel (measuring grid) a, b, c



Applying the Wheatstone Bridge Circuit




1			$\varepsilon = \varepsilon_n + \varepsilon_b = \frac{4}{k} \cdot \frac{U_A}{U_B} - \varepsilon_\vartheta$ <table border="1"> <thead> <tr> <th>T</th><th>F</th><th>M_b</th><th>M_d</th></tr> </thead> <tbody> <tr> <td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	T	F	M _b	M _d	1	1	1	0
T	F	M _b	M _d								
1	1	1	0								
2			$\varepsilon = \varepsilon_n + \varepsilon_b = \frac{4}{k} \cdot \frac{U_A}{U_B}$ <table border="1"> <thead> <tr> <th>T</th><th>F</th><th>M_b</th><th>M_d</th></tr> </thead> <tbody> <tr> <td>0</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	T	F	M _b	M _d	0	1	1	0
T	F	M _b	M _d								
0	1	1	0								
3			$\varepsilon = \varepsilon_n + \varepsilon_b = \frac{1}{(1+\mu)} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$ <table border="1"> <thead> <tr> <th>T</th><th>F</th><th>M_b</th><th>M_d</th></tr> </thead> <tbody> <tr> <td>0</td><td>1+μ</td><td>1+μ</td><td>0</td></tr> </tbody> </table>	T	F	M _b	M _d	0	1+μ	1+μ	0
T	F	M _b	M _d								
0	1+μ	1+μ	0								
4			$\varepsilon = \varepsilon_b = \frac{1}{2} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$ <table border="1"> <thead> <tr> <th>T</th><th>F</th><th>M_b</th><th>M_d</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>2</td><td>0</td></tr> </tbody> </table>	T	F	M _b	M _d	0	0	2	0
T	F	M _b	M _d								
0	0	2	0								

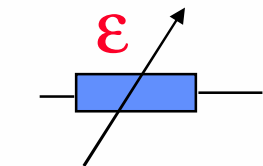

active strain gauge





passive strain gauge or resistor

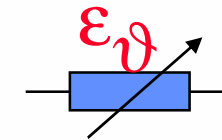

strain gauge for temperature compensation



M_b-bending moment; M_d-torque; T-temperature; F-normal force

Applying the Wheatstone Bridge Circuit

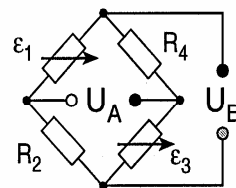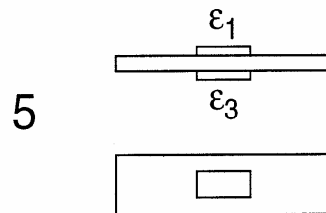



$$\varepsilon = \varepsilon_n = \frac{1}{2} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B} - \varepsilon_0$$

T	F	M _b	M _d
2	2	0	0

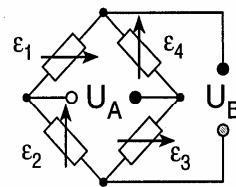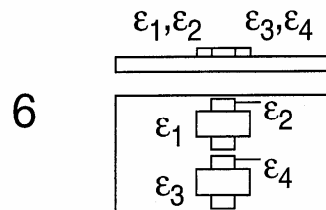



$$\varepsilon = \varepsilon_n + \varepsilon_b = \frac{1}{2(1+\mu)} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$

T	F	M _b	M _d
0	2(1+μ)	2(1+μ)	0

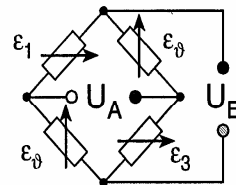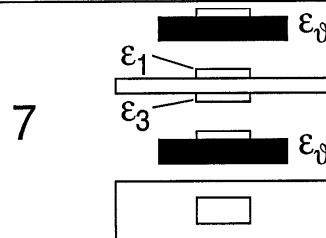

$$\varepsilon = \varepsilon_n = \frac{1}{2} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$


T	F	M _b	M _d
0	2	0	0

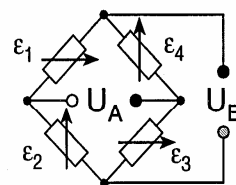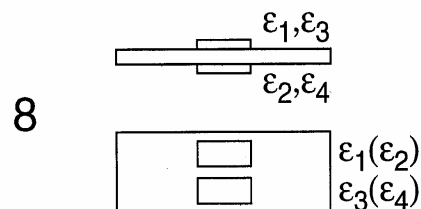

$$\varepsilon = \varepsilon_b = \frac{1}{4} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$


T	F	M _b	M _d
0	0	4	0

Applying the Wheatstone Bridge Circuit

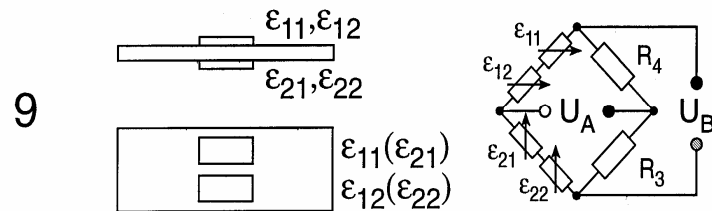


$$\varepsilon = \varepsilon_b = \frac{1}{2} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$

T	F	M _b	M _d
0	0	2	0

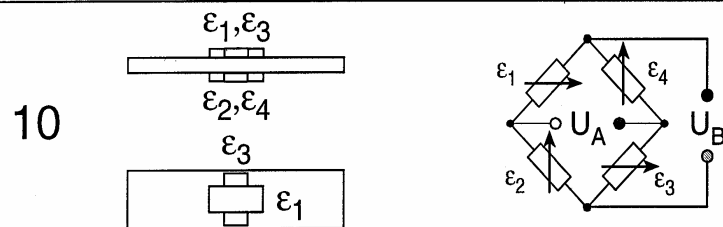


$$\varepsilon = \varepsilon_b = \frac{1}{2(1-\mu)} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$

T	F	M _b	M _d
0	0	2(1-μ)	0

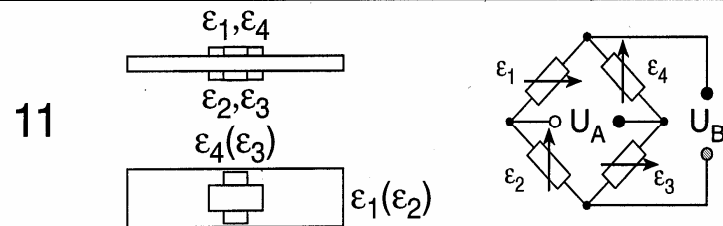

$$\varepsilon = \varepsilon_b = \frac{1}{2(1+\mu)} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$


T	F	M _b	M _d
0	0	2(1+μ)	0

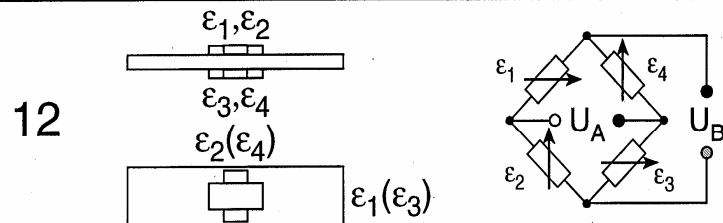

$$\varepsilon = \varepsilon_n = \frac{1}{2(1+\mu)} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$


T	F	M _b	M _d
0	2(1+μ)	0	0

Applying the Wheatstone Bridge Circuit

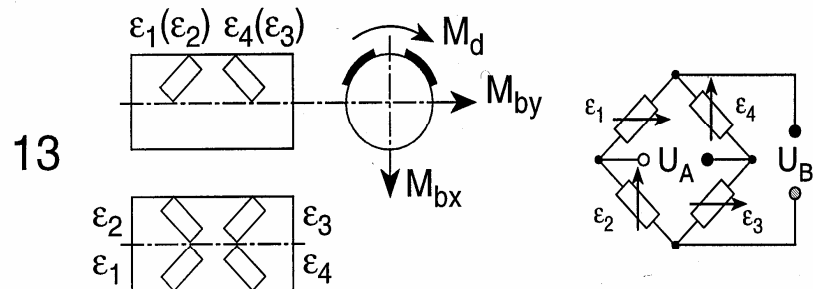


$$\varepsilon = \varepsilon_d = \frac{1}{4} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$

T	F	M _{bx}	M _{by}	M _d
0	0	0	0	4

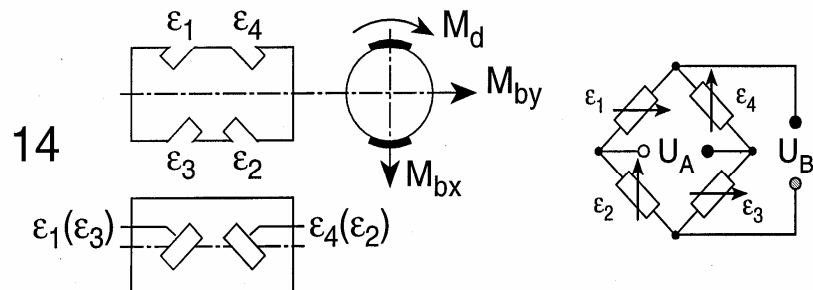

$$\varepsilon = \varepsilon_d = \frac{1}{4} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$

T	F	M _{bx}	M _{by}	M _d
0	0	0	0	4

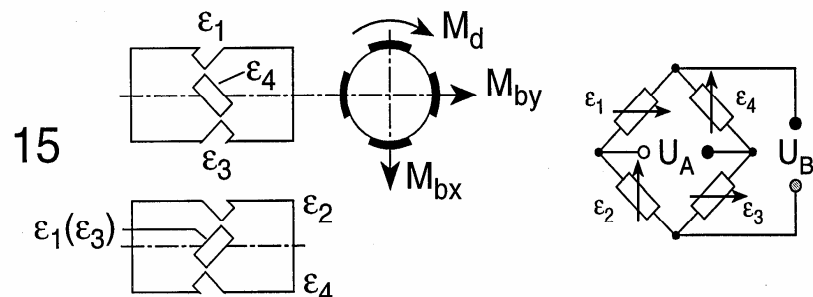

$$\varepsilon = \varepsilon_d = \frac{1}{4} \cdot \frac{4}{k} \cdot \frac{U_A}{U_B}$$

T	F	M _{bx}	M _{by}	M _d
0	0	0	0	4

Reduction and elimination of measurement errors, especially temperature effects

- *temperature error can be corrected mathematically*
- temperature compensation using Wheatstone bridge circuit
 - quarter bridge with compensating strain gauge
 - half and full bridges

Basics


Every strain gauge gives out a value when the temperature varies – without any mechanical load.

Cause:

- Work piece expansion with temperature
- Change in specific resistance of strain gauge
- Strain gauge grid expansion with temperature

Basics

Thermal output of a quarter bridge

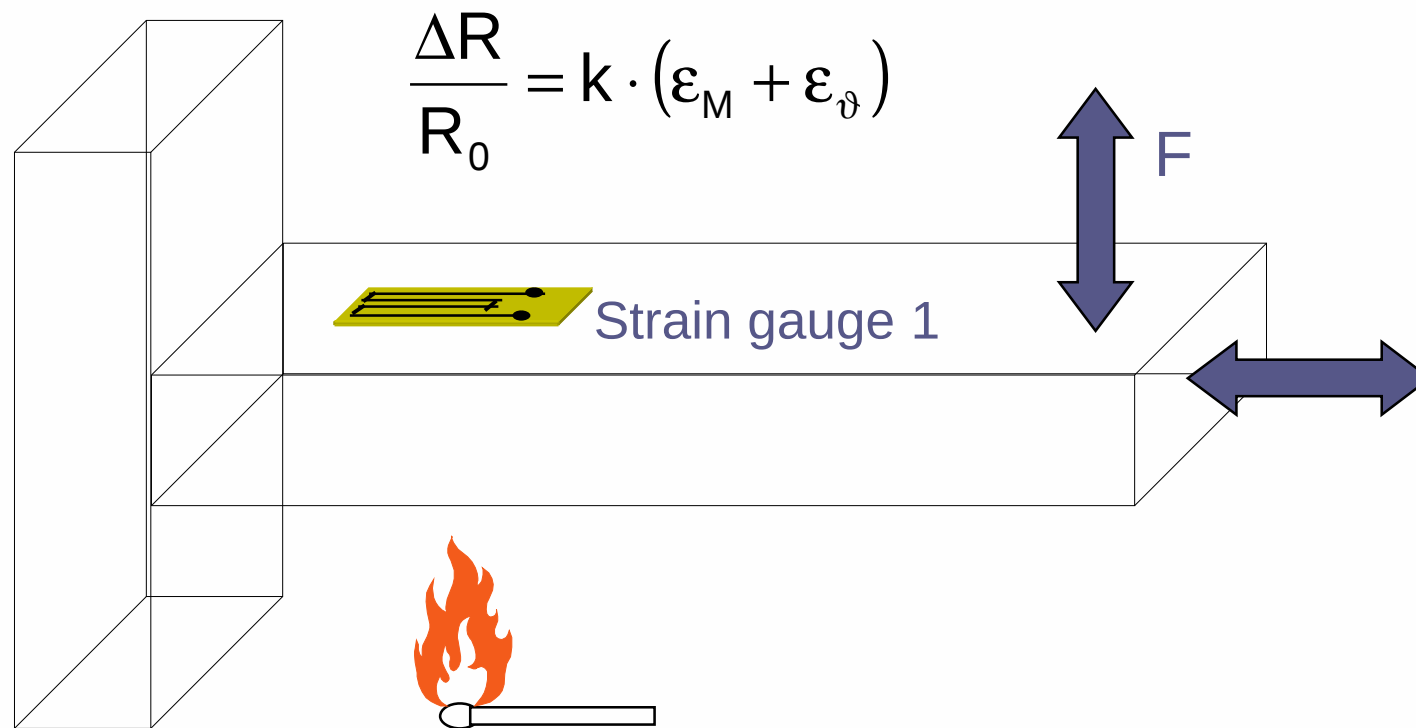

Temperature compensated strain gauges (series Y)

1	for ferritic steel	$\alpha = 10,8 \cdot 10^{-6} / \text{K}$
3	for aluminium	$\alpha = 23 \cdot 10^{-6} / \text{K}$
5	for austenitic steel	$\alpha = 16 \cdot 10^{-6} / \text{K}$
6*	for quartz	$\alpha = 0,5 \cdot 10^{-6} / \text{K}$
7*	for titanium /grey cast iron	$\alpha = 9 \cdot 10^{-6} / \text{K}$
8*	for plastic material	$\alpha = 65 \cdot 10^{-6} / \text{K}$
9*	for molybdenum	$\alpha = 5,4 \cdot 10^{-6} / \text{K}$

* not for all measuring grid length available

Applying the Wheatstone Bridge Circuit



Dehnungsmeßstreifen
Strain Gauges
Jauges d'extensométrie

Typ **6/120LY11**
US-Type

Stückzahl
Quantity
Quantité **10**


mit ☐ ohne ☒
with without
avec sans

Applikationshilfe
Application aid
Support d'aide à l'application

Widerstand Resistance Résistance	120 [Ω]	+ 0.35	[%]	Temperaturkoeffizient des k-Faktors Temperature coefficient of gauge factor	104 ± 10	[10 ⁻⁶ /°C]
k-Faktor Gauge factor Facteur k	2,08 ± 1	- 0.35	[%]	Coefficient de température du facteur k	(-10 ... +45 °C)	
Querempfindlichkeit Transverse Sensitivity Sensibilité transverse		-0.1	[%]	Artikel Nr. Part No. No. de Réf.	1-LY11-6/120	
		-	[%]	Folienlos Lot Lot de la feuille	A251/16/01	
Temperaturkompensation: Angepaßt für Temperature Compensation: Compensated for Compensation de température: Compensé pour				Herstellungslös Batch Lot de fabrication	833351/02	

$\alpha = 10.8 [10^{-6} / ^\circ\text{C}]$

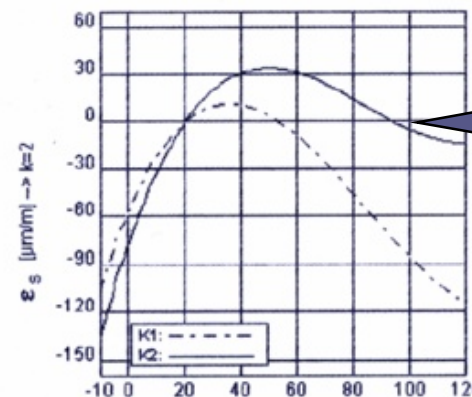☒ Stahl
Steel
Acier
 ☐ Alumi-
num
 ☐ Sonstige
Other
Autre



$\epsilon_s(T) = -57.1 + 4.15 T - 7.32 \cdot 10^{-2} T^2 + 2.89 \cdot 10^{-4} T^3 + 0.0333 \cdot L \cdot (T-20) \mu\text{m/m} \pm 0.3 (\mu\text{m/m}) \cdot ^\circ\text{C}^{-1}$


HOTTINGER BALDWIN
HBW MÄSSTECHNIK GMBH
693 Darmst
Tel.: +49 1805-22 32 49; Telefax: +49 1805-22 32 49
<http://www.hbmwt.com>

Temperature Compensation
(Material, thermal expansion coefficient)


remaining temperature variation

polynomial (of the remaining
temperature variation)
so that the arising measurement fault
can be corrected mathematically

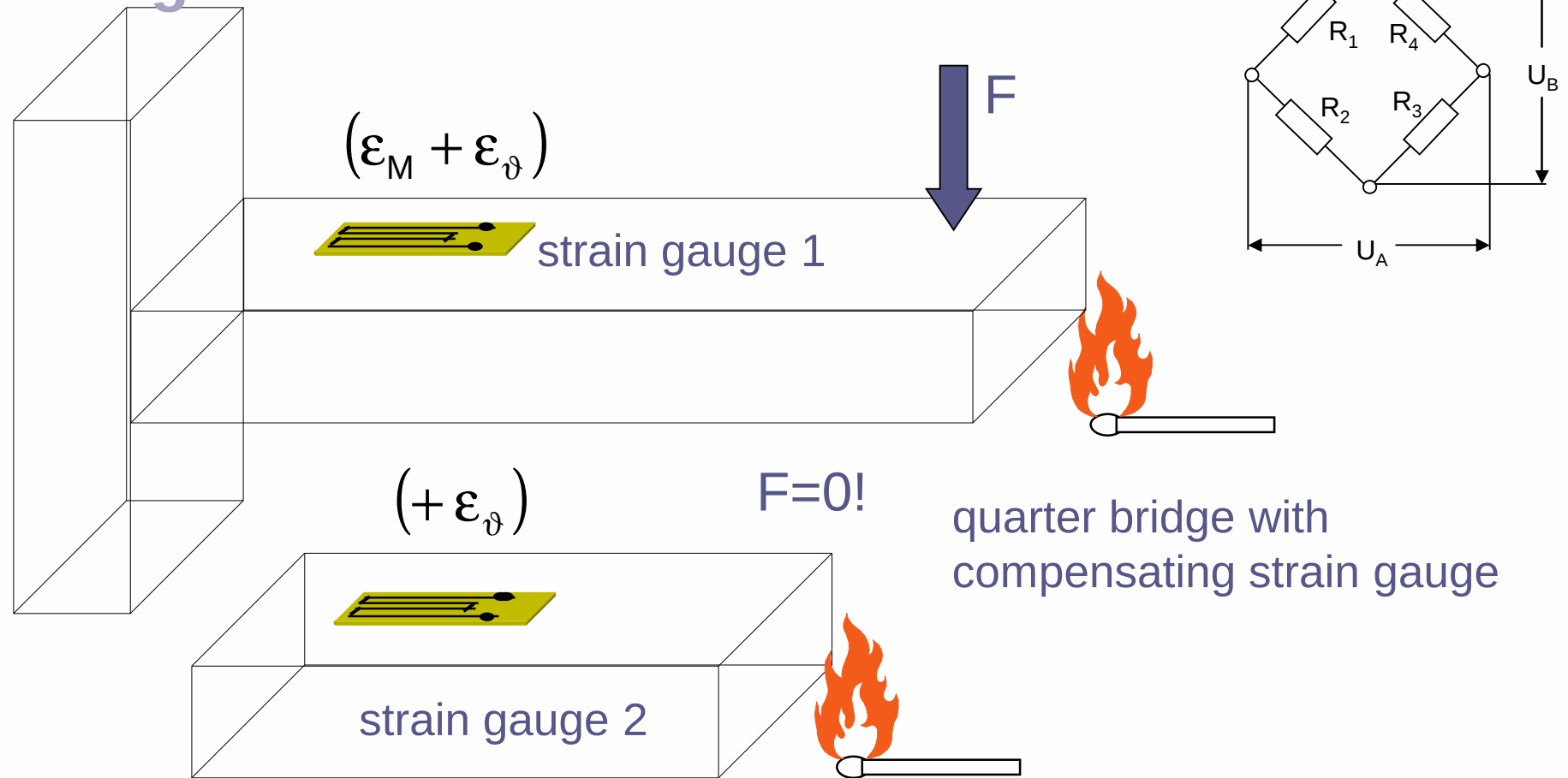temperature compensation using Wheatstone bridge circuit



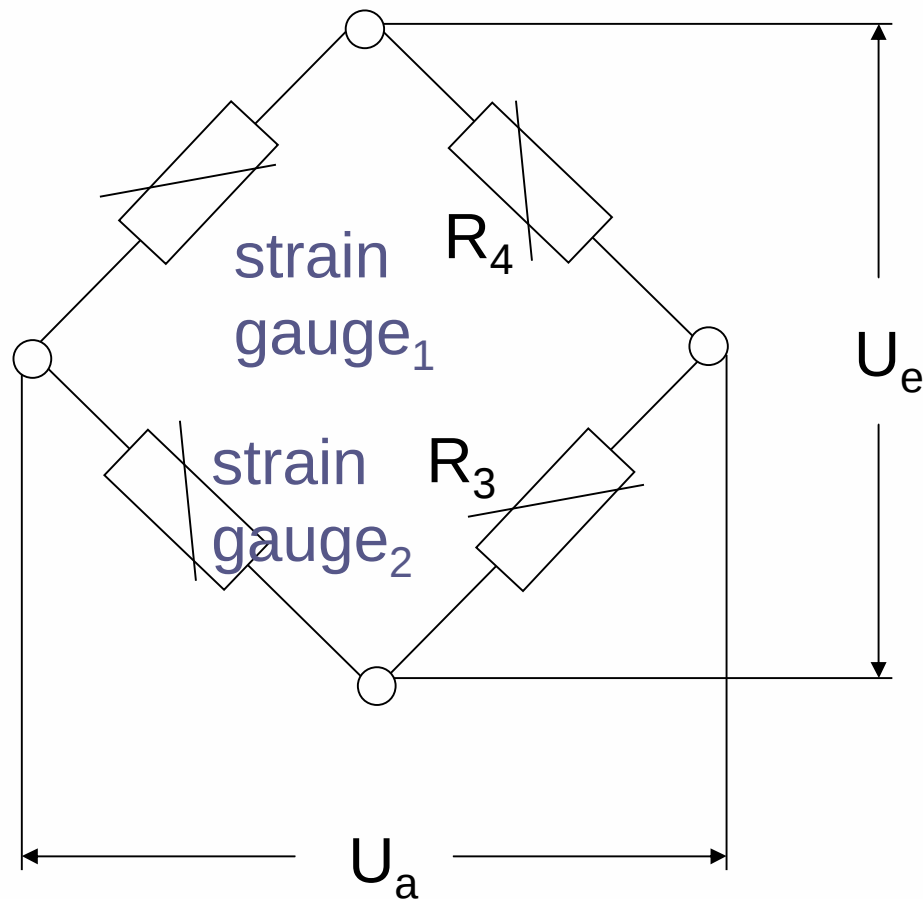temperature compensation using Wheatstone bridge circuit



quarter bridge with
compensating strain gauge

$$\text{strain gauge}_1 \Rightarrow (\varepsilon_M + \varepsilon_{\vartheta})$$

$$\text{strain gauge}_2 \Rightarrow (+\varepsilon_{\vartheta})$$

$$\frac{U_a}{U_e} = \frac{k}{4} (\varepsilon_1 - \varepsilon_2)$$

quarter bridge with compensating strain gauge

The compensating strain gauge:

- must be applied in a spot where it will be subjected to the same interference effect as the active strain gauge
- must have the same physical properties as the active strain gauge (same package or batch)
- must only be subjected to the interference effect and never to the quantity to be measured ε_M or its side effects
- must be applied at the same material (e.g. steel) as the active strain gauge



temperature compensation using Wheatstone bridge circuit

Advantages:

- it is not necessary to measure the temperature during the strain measurement
- it is not absolutely necessary that the strain gauges are adjusted to the material

temperature compensation using Wheatstone bridge circuit

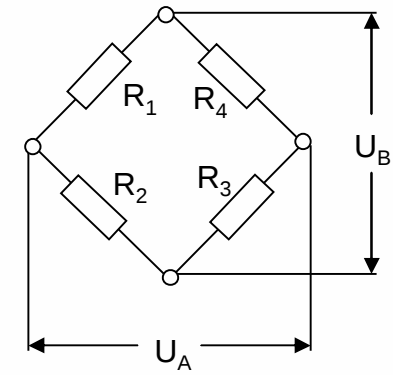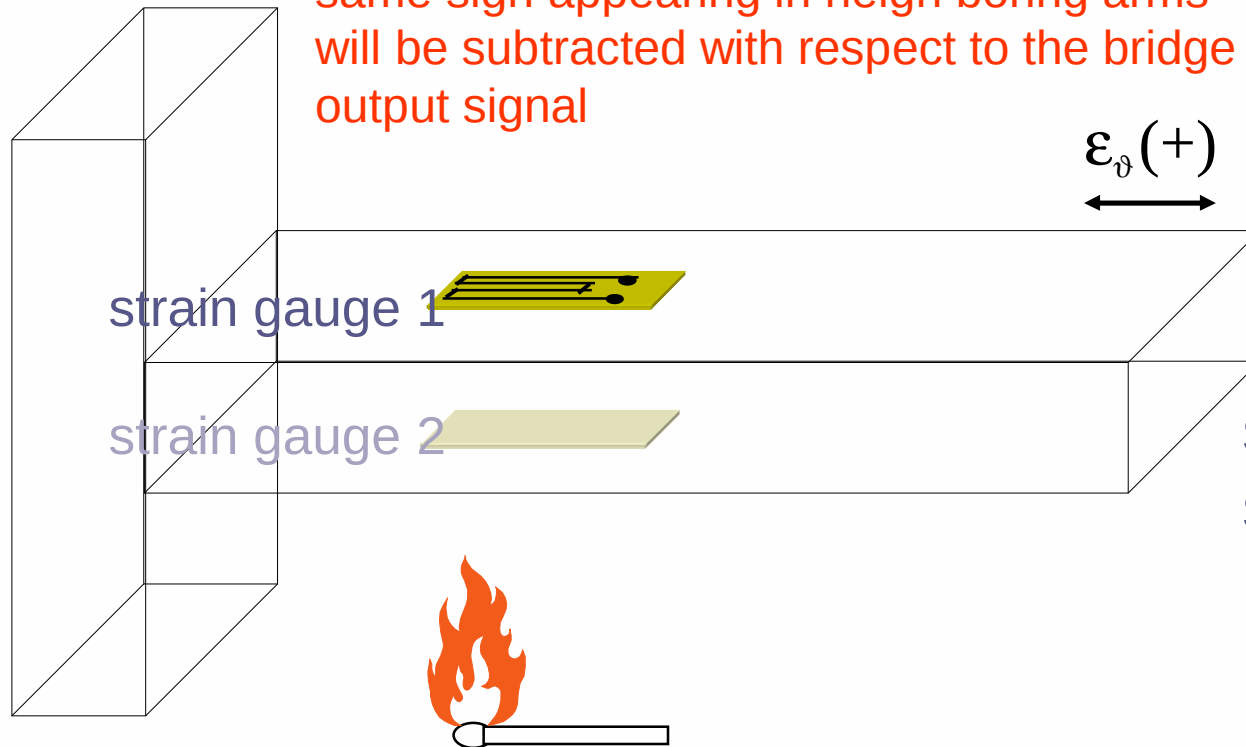Changes of the strain gauge resistance of the same sign appearing in neighboring arms will be subtracted with respect to the bridge output signal





strain gauge 1: +
strain gauge 2: +


half bridge

temperature compensation using Wheatstone bridge circuit

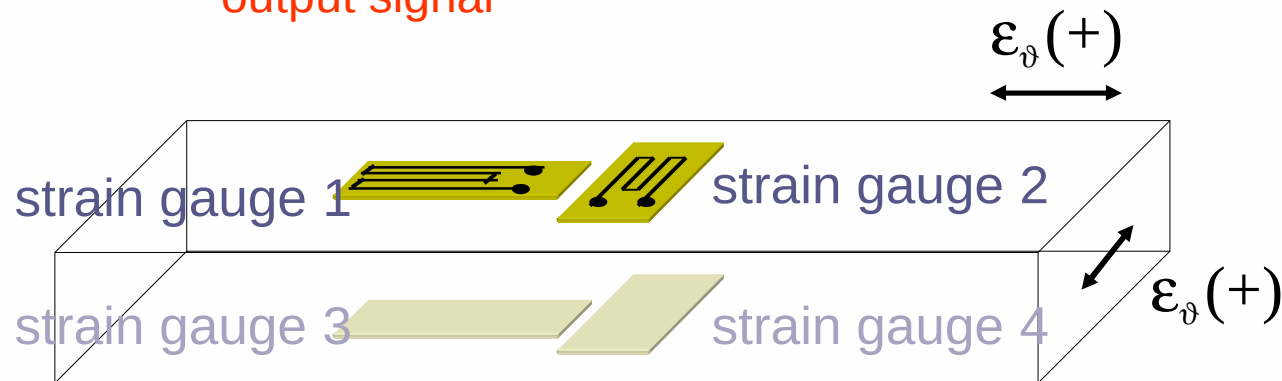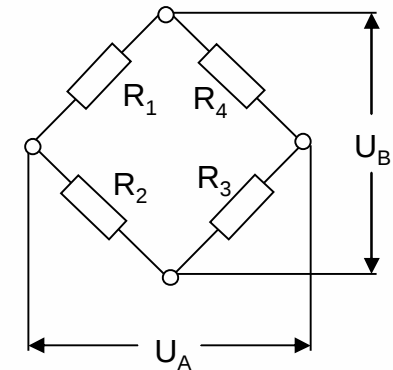Changes of the strain gauge resistance of the same sign appearing in neighboring arms will be subtracted with respect to the bridge output signal



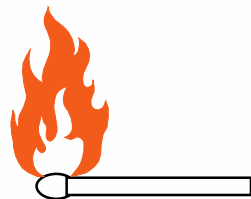s. g. 1: +
s. g. 2: +
s. g. 3: +
s. g. 4: +



full bridge

thank you...
... for your attention

Hottinger Baldwin Messtechnik GmbH
Im Tiefen See 45
D-64293 Darmstadt

www.hbm.com

Dirk Eberlein
Tel. 06151/803-763
dirk.eberlein@hbm.com



measurement with confidence